
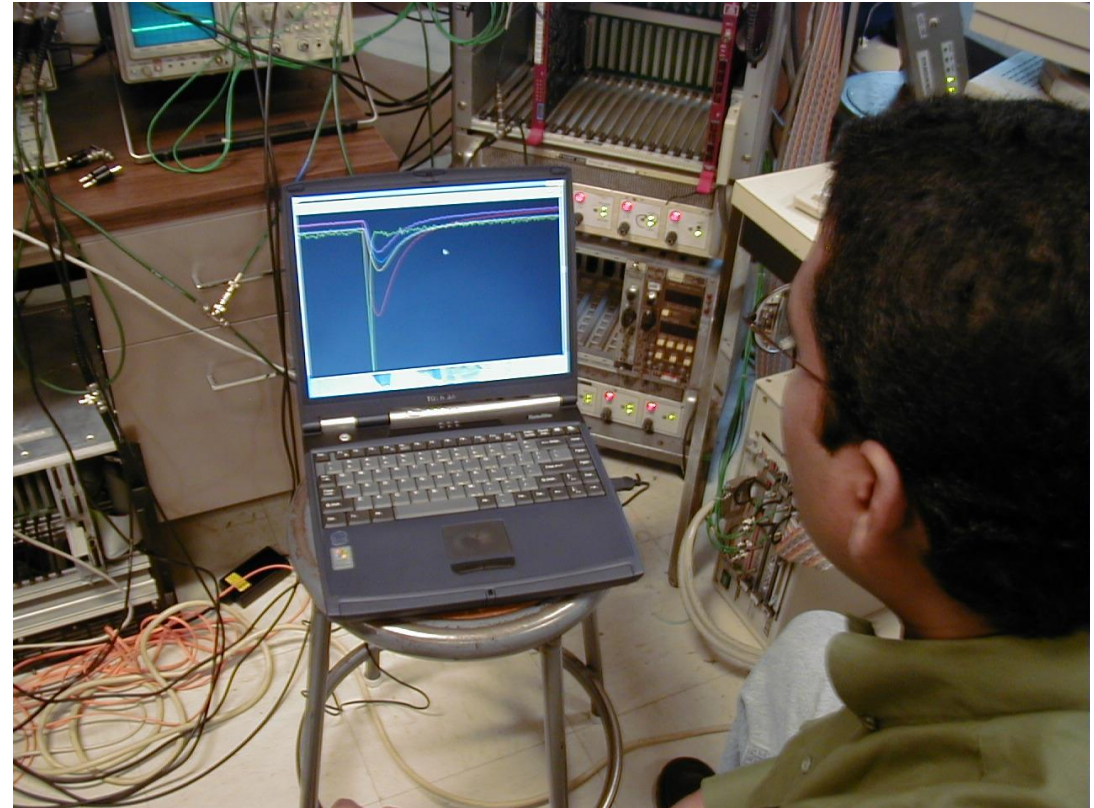


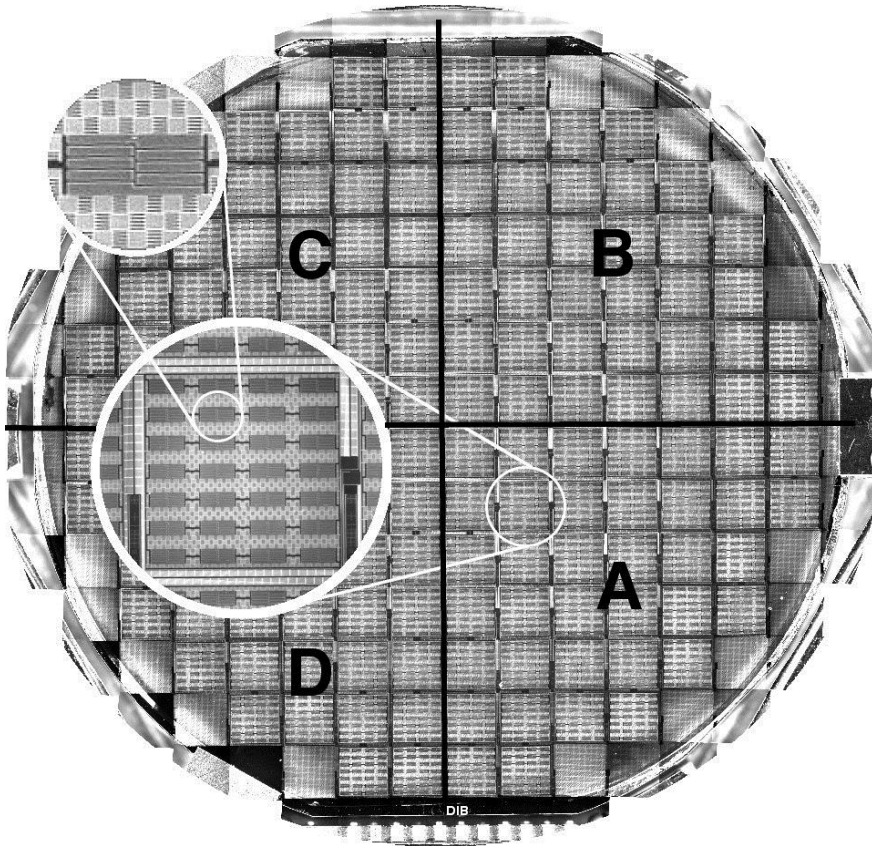
Understanding the CDMS detectors: Choose a power supply for your TES



Outline

- Energy deposition in CDMS detectors
- Sensing the energy deposition
 - Transition Edge Sensor (TES)
 - Making the TES human-readable: the TES circuit I
 - Keeping the TES working: the TES circuit II
 - Requirements on circuit stability: the TES circuit III
 - Using an off-the-shelf current source: the TES circuit IV

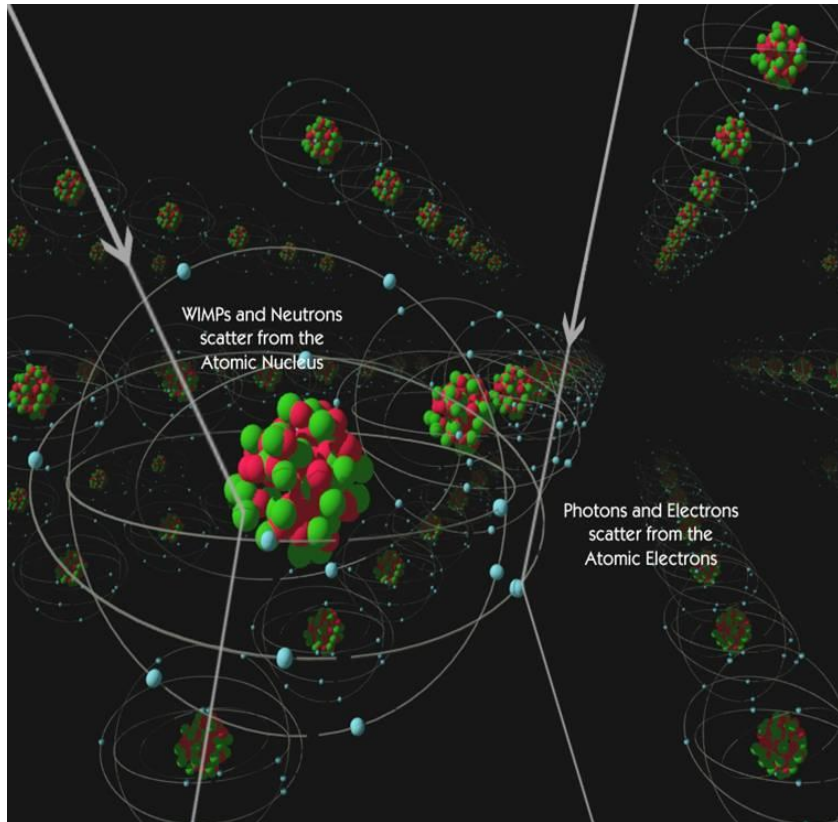Energy deposition: an energetic particle interacts within the CDMS crystal



At the moment of the interaction

A particle can deposit energy in a CDMS crystal in two ways:

1. Create phonons (vibrations in the crystal lattice)
2. Create ionization (electron-hole pairs)

Slightly after the interaction




More phonons: if the electrons and holes feel an electric field, they'll accelerate and produce more phonons via the Luke-Neganov effect.

A lucky break

A particle interacting with the detector has two options: (1) interact with a nucleus and (2) interact with an electron.

When a particle interacts with a nucleus, the energy preferentially goes into phonon creation; with an electron interaction, the energy preferentially goes to ionization.

See the energy

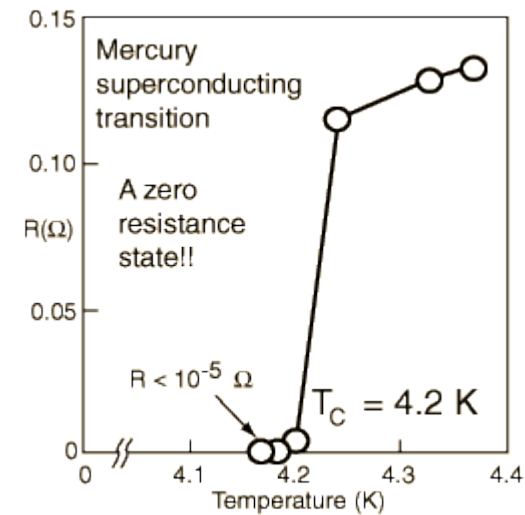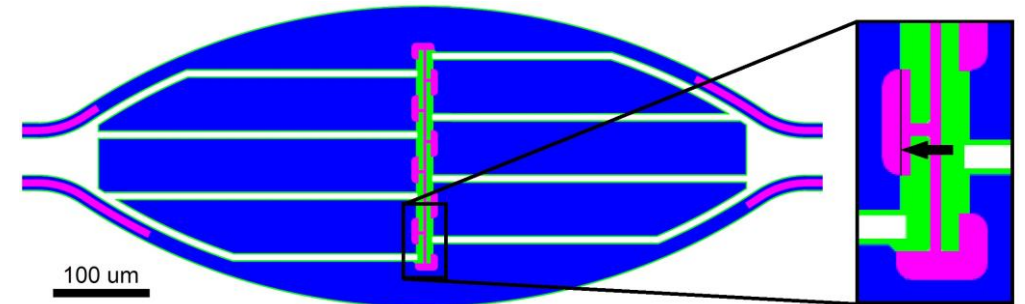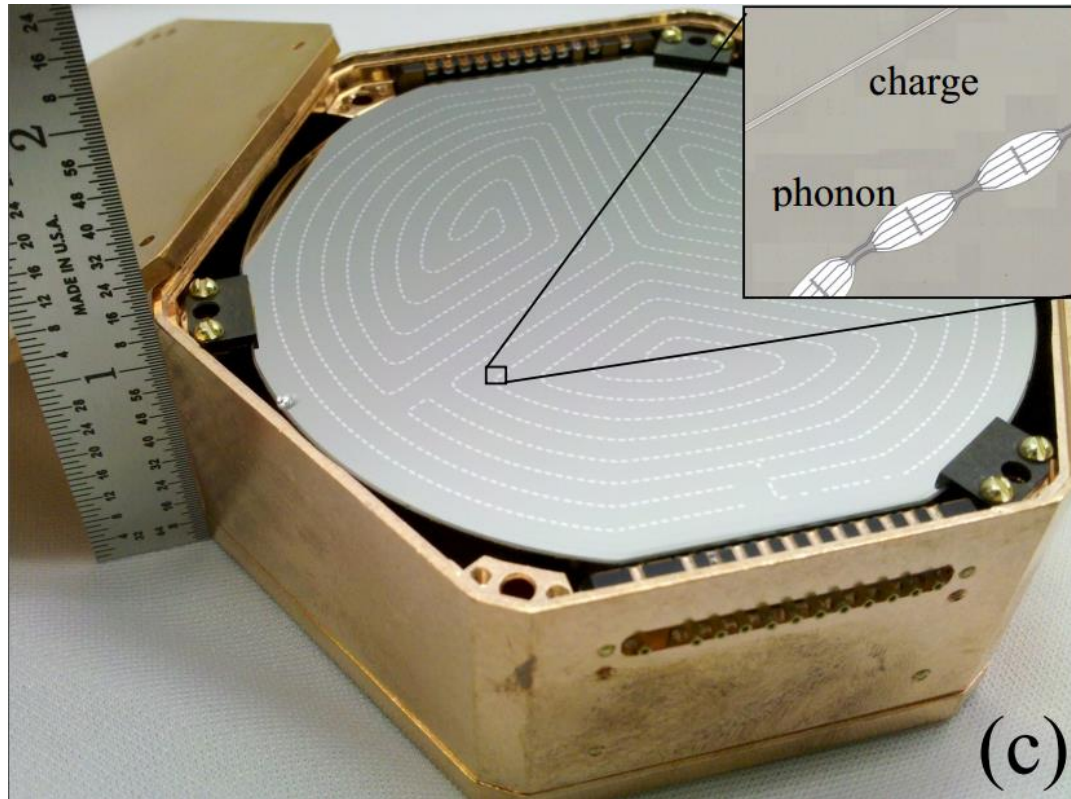


Deposit energy
 \Rightarrow Increase TES temperature
 \Rightarrow Increase TES resistance

See the energy



▽ We can use SQUIDS to see magnetic fields with very little added noise

The TES is on the crystal

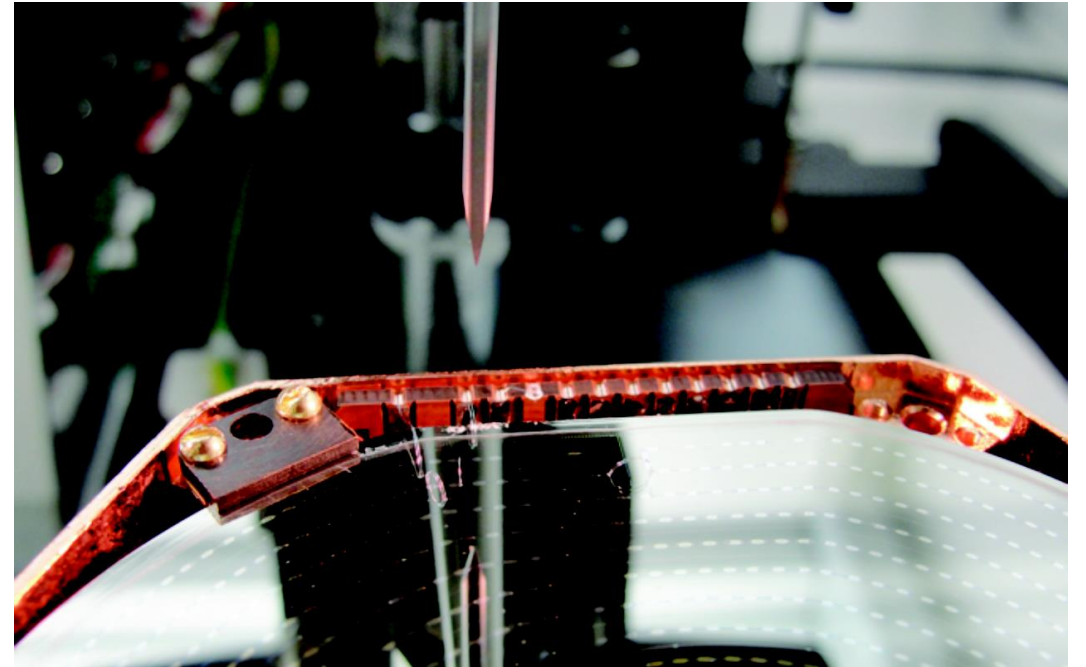

See the energy **for multiple events**



$$P = I^2 R$$

$$\delta P = 2IR\delta I + I^2\delta R$$

is $\delta P < 0$?


in this circuit the voltage is constant

$$\delta V = I\delta R + R\delta I = 0$$

$$\delta P = -2I^2\delta R + I^2\delta R$$

$$= -I^2\delta R$$

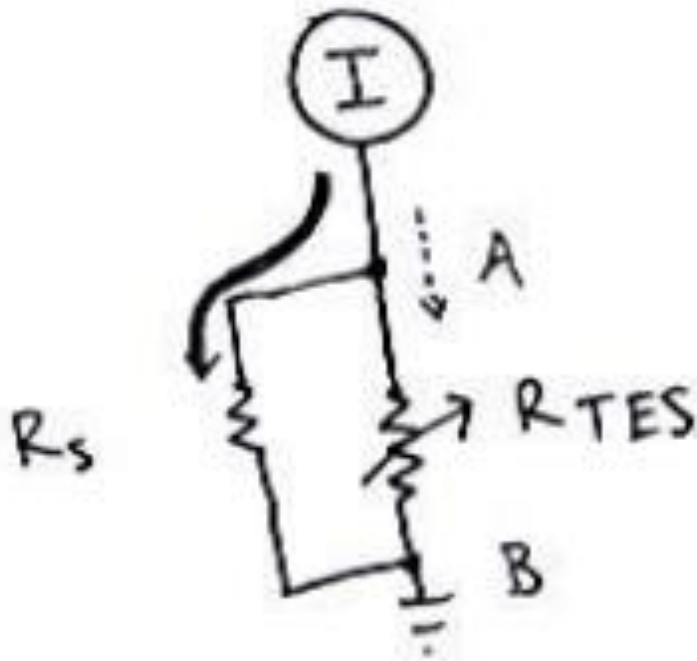
See the energy with existing power-supply technology



$$\begin{aligned} V_{AB} &= I_{TES} R_{TES} = I_s R_s \\ V_{AB} &= \left(I \times \frac{R_{TES}}{R_s + R_{TES}} \right) \times R_s \\ &\quad \quad \quad I_s \\ &= I R_s \times \frac{1}{1 + R_s / R_{TES}} \end{aligned}$$

The TES (one channel = an array of sensors hooked up in parallel) ends up being ~ 2 Ohms.
The shunt resistor is ~ 20 milli Ohms.

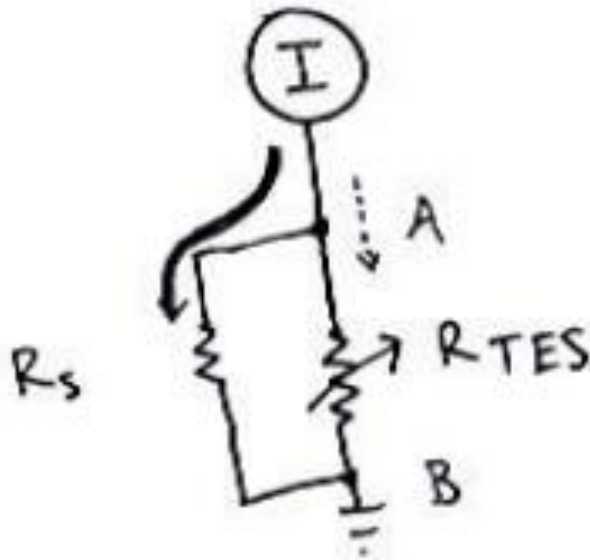See the energy with existing power supply technology



$$I_{TES} = V_{AB} / R_{TES} \approx I \frac{R_s}{R_{TES}}$$
$$\delta I_{TES} = \left(\frac{R_s}{R_{TES}} \delta I \right) \approx \frac{I R_s}{R_{TES}^2} \delta R_{TES}$$

current source fluctuations

physics on the crystal

The TES (one channel = an array of sensors hooked up in parallel) ends up being ~ 2 Ohms.

The shunt resistor is ~ 20 milli Ohms.

Heating the TES into its superconducting transition typically requires ~ 20 micro Amps.